

### Introduction:

A voltage-controlled oscillator (VCO) is an electronic oscillator whose oscillation frequency is controlled by a voltage input. The applied input voltage determines the instantaneous oscillation frequency. Consequently, a VCO can be used for frequency modulation (FM) or phase modulation (PM) by applying a modulating signal to the control input.

A VCO is also an integral part of a phase-locked loop. VCOs are used in synthesizers to generate a waveform whose pitch can be adjusted by a voltage determined by a musical keyboard or other input. A voltage-to-frequency converter (VFC) is a special type of VCO designed to be very linear in frequency control over a wide range of input control voltages.

A Voltage-Controlled Oscillator (VCO) is an essential element in contemporary electronic systems, especially in communication, signal processing, and control uses. Its main role is to produce an oscillating signal where the frequency is regulated by an input voltage, allowing for adaptive frequency modification. VCOs are fundamental to Phase-Locked Loops (PLLs), which are extensively utilized in frequency synthesis, clock generation, and demodulation within communication frameworks. They act as local oscillators in RF transceivers, facilitating frequency transformation in both superheterodyne and direct-conversion designs. Furthermore, VCOs are crucial in frequency modulation (FM) and spread spectrum communication systems, including GPS and CDMA, improving signal integrity and diminishing interference. Their rapid response, extensive tuning range, and potential for integration render them suitable for uses that demand exact frequency control, such as microprocessor clock generation and dynamic system regulation. In addition, performance metrics such as phase noise, tuning range, and linearity are vital in assessing the effectiveness and dependability of VCOs in these roles.


VCOs are used in function generators, phase-locked loops including frequency synthesizers used in communication equipment and the production of electronic music, to generate variable tones in synthesizers.

VCOs play a crucial role in a phase-locked loop (PLL), which is a control system that produces a signal with a constant relationship to the phase of a "reference" signal. PLLs are utilized extensively in radio, telecommunications, computers, and various other electronic applications. VCOs can additionally serve other purposes in frequency and phase modulation, and they find applications in areas like function generators and synthesizers.

### Background theory:

A Voltage-Controlled Oscillator (VCO) is an electronic oscillator whose output frequency is determined by an input control voltage. It is widely used in applications where the output frequency needs to be adjusted dynamically in response to changing conditions or input signals.

### Block diagram:

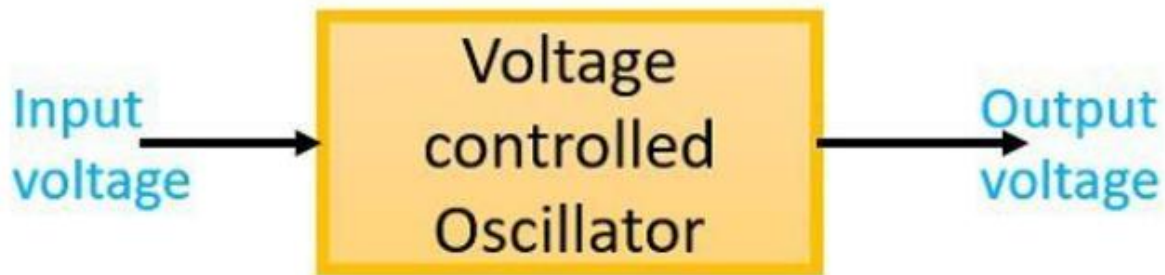

VCO generates an output signal having an adjustable frequency range that is controlled by the dc input voltage. It is a type of oscillator in which the output frequency obtained is the function of the input signal. Usually, the frequency of an oscillator is measured by RC time constant. However, there exist some applications where the frequency is to be controlled by the input voltage.

VCOs play a crucial role in a phase-locked loop (PLL), which is a control system that produces a signal with a constant relationship to the phase of a "reference" signal. PLLs are utilized extensively in radio, telecommunications, computers, and various other electronic applications. VCOs can additionally serve other purposes in frequency and phase modulation, and they find applications in areas like function generators and synthesizers.

### Working Principle of Voltage Controlled Oscillator (VCO)


There are numerous varieties of VCO circuits; a fundamental one can be created by simply using a capacitor, an inductor, and a resistor to form a tank circuit. Additionally, Op-Amps, Multivibrators, transistors, and 555 timers can be employed to create oscillating circuits. Furthermore, there are specialized IC packages such as LM566 and LM567, among others, which can function as VCOs. To grasp the fundamental concept of a VCO, let us examine an RC oscillator.

VCO can be in the form of either LC, crystal oscillator, RC oscillator or Multivibrator.

In a **RC oscillator** the frequency of the output wave depends on the value of the capacitor used in the circuit, since the frequency is given by the formulae

$$f = \frac{1}{2\pi RC}$$

Hence in this case the frequency of oscillation is inversely proportional to the value of capacitance used in the circuit. So now to control the output frequency and to make it work as a VCO we have to vary the capacitance of the Capacitor based on the value of the Input voltage. This can be achieved with the help of varactor diodes. These diodes change the value of capacitance across them based on the voltage applied. A sample output graph of a VCO is shown below.

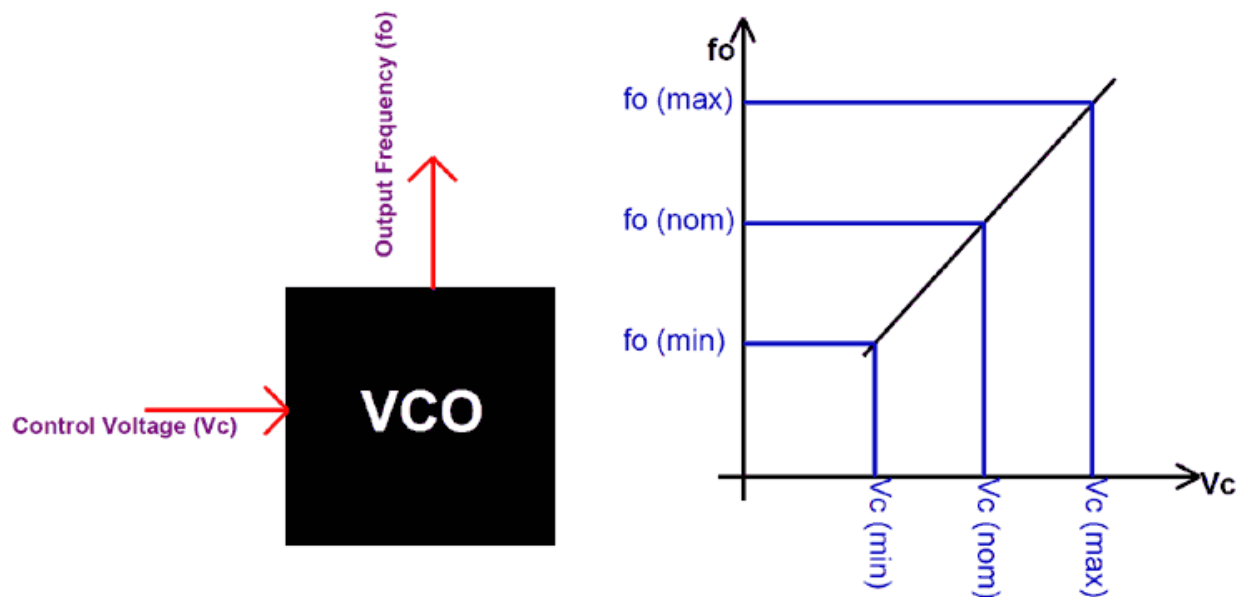

The control voltage to be  $V_c$  and the output frequency as  $f_o$ . Then under normal operating condition a nominal voltage provided to the VCO for which a nominal Frequency is produced by the VCO. As the input voltage (control voltage) is increased the output frequency increases and the vice versa is also possible.

In case of an LC type oscillator, the frequency is given as

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Thus, any increase in the control voltage will resultantly decrease the capacitance. This decrease in capacitance will ultimately increase the frequency of the system.

In a VCO, the oscillator runs at its usual frequency on applying nominal control voltage  $V_c$ . The frequency of the oscillator increases with the increase in  $V_c$  above nominal and decreases with the decrease in  $V_c$  below nominal.

### Types of Voltage Controlled Oscillators


There are many types of VCO circuits used in different applications, but they can be broadly classified into two types based on their output voltage.

**Harmonic Oscillators:** If the Output waveform of the oscillator is sinusoidal then it is called as harmonic Oscillators. The RC, LC circuits and Tank circuits fall into this category. These types of oscillators are harder to implement but they better stability than the Relaxation Oscillator. Harmonic oscillators are also called as linear voltage Controlled oscillator.

**Relaxation Oscillator:** If the output waveform of the oscillator is in sawtooth or triangular form then the oscillator is called as Relaxation Oscillator. These are comparatively easy to implement and hence most widely used. Relaxation Oscillator can further be classified as

- Emitter Coupled Voltage Controlled Oscillator
- Grounded capacitor Voltage Controlled Oscillator
- Delay based ring Voltage Controlled Oscillator


### Schematic cell view:

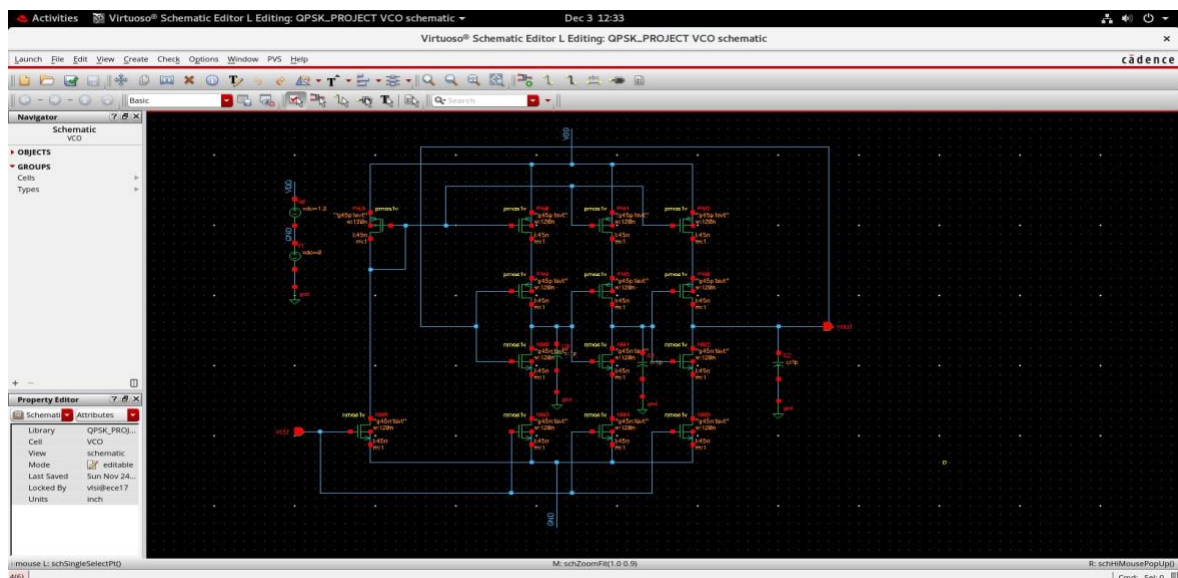

## Implementation of VCO using cadence

The above schematic is Voltage-Controlled Oscillator (VCO) created in Cadence Virtuoso, probably utilizing a differential or ring oscillator architecture. The circuit is made up of several stages of transistors positioned symmetrically, indicating a differential structure intended to produce stable oscillations. These transistors, along with resistive and capacitive elements, constitute the fundamental oscillation circuit. The oscillation frequency is regulated by a control voltage ( $V_{ctr}$ ), which modifies the current or the capacitance within the circuit, facilitating frequency modulation. This control system permits dynamic adjustment of the output frequency, rendering the VCO appropriate for uses such as frequency synthesis in Phase-Locked Loops (PLLs) or RF communication systems. The symmetrical configuration guarantees minimized phase noise and improved stability, which are essential for high-performance applications. Feedback is employed to sustain consistent oscillations by fulfilling the Barkhausen criterion. The output is probably taken from one of the nodes, supplying an oscillatory signal that may be further utilized in signal processing or modulation activities.

### Test circuit:

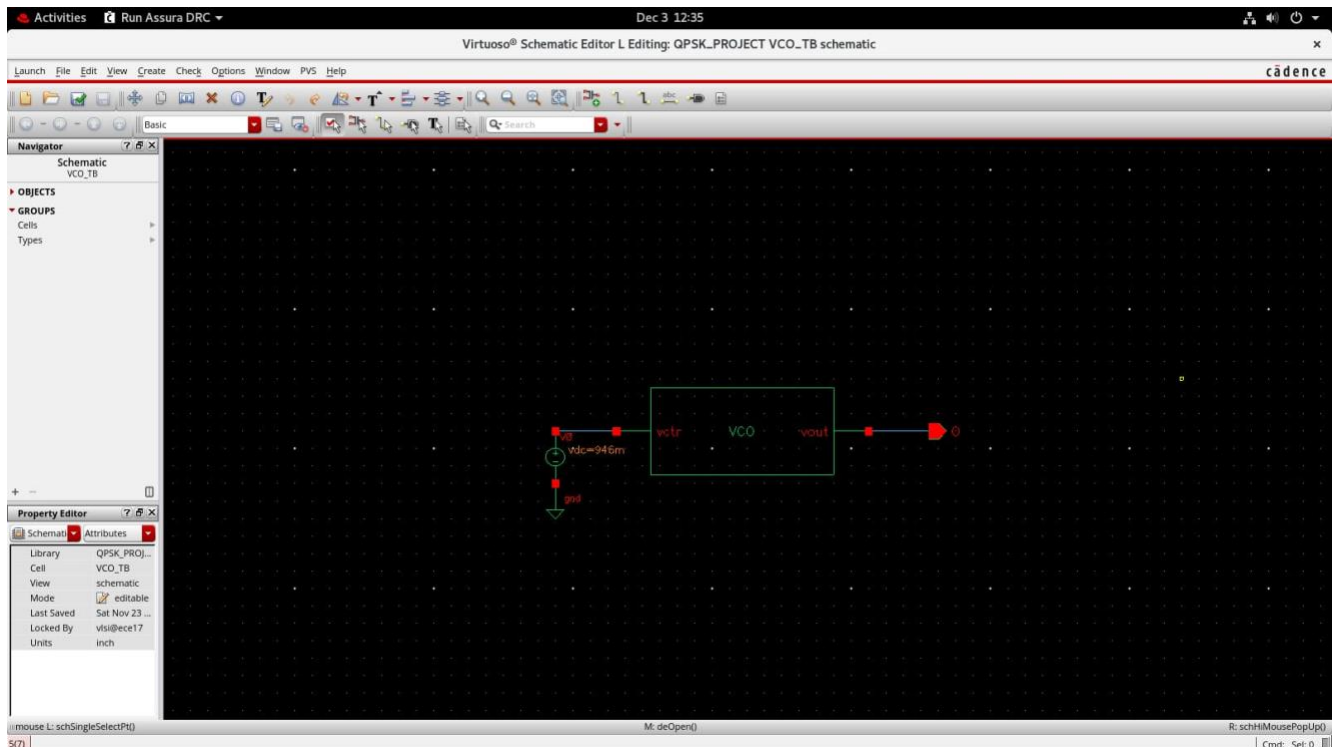

## Implementation of VCO using cadence


The above schematic illustrates a testbench circuit intended for assessing the performance of a Voltage-Controlled Oscillator (VCO) in Cadence Virtuoso. This configuration contains a DC voltage source named "Vctrl," which delivers a control voltage of 0 to 2V to the VCO.

The control voltage acts as the input signal that modulates the oscillation frequency of the VCO. By adjusting this voltage, the testbench facilitates dynamic adjustment of the output frequency. The VCO block features two primary ports: the Vctrl input that accepts the control voltage and the Vout output that generates the oscillating signal.

The ground connection provides a common reference point for the entire circuit. The output node (Vout) is employed to observe the oscillatory signal, permitting analysis of its frequency, amplitude, and phase characteristics. This testbench is crafted to confirm essential performance metrics such as the frequency tuning range, phase noise, and oscillation stability, ensuring that the VCO adheres to design specifications.

Additionally, the testbench helps evaluate the linearity of the VCO, ensuring a consistent frequency response to varying control voltages. This setup is crucial for validating the VCO's performance in applications like phase-locked loops (PLLs) and frequency synthesizers.

### Result and Discussion:

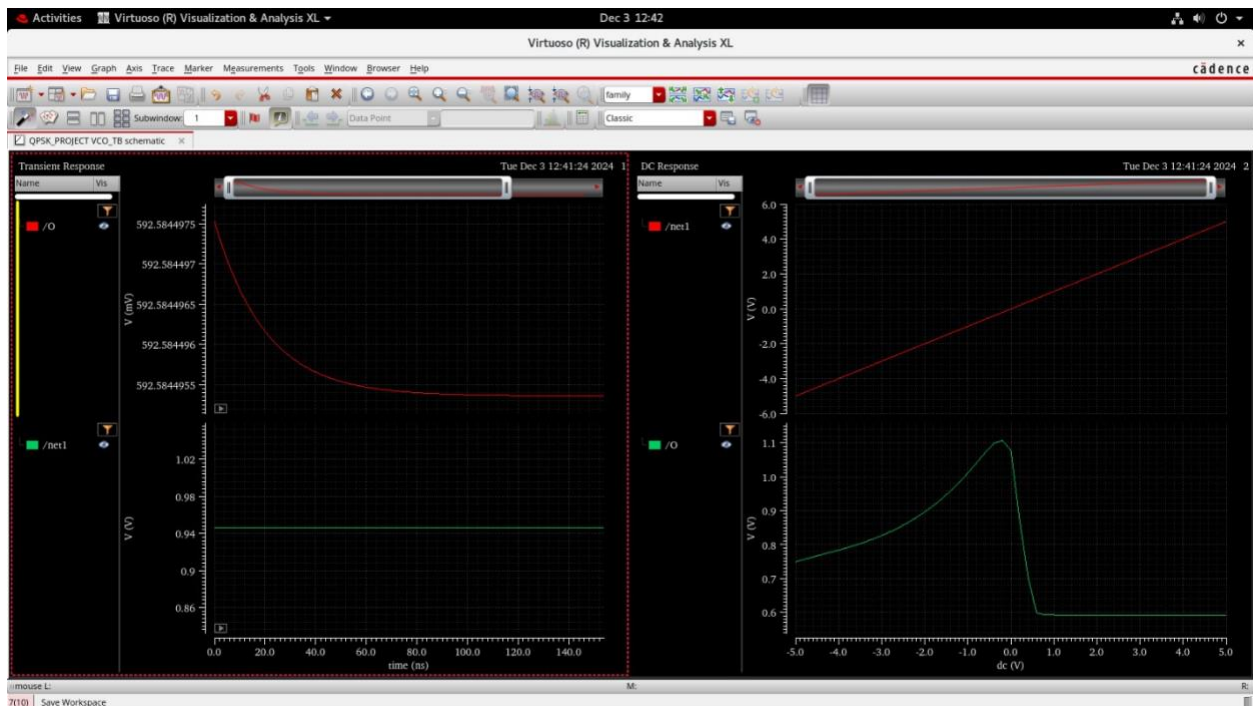



### Transient response:

The plot on the left depicts the signal's behavior from 0 to 150 ns. At first, the output exhibits a sharp variation, signaling a transient response as the circuit stabilizes. After some time, the output voltage seems to stabilize at a constant value, indicating the steady-state oscillation of the VCO. The red curve in the top graph signifies the time-domain response of the output voltage, depicting an oscillation that ultimately achieves a stable voltage level. The lower graph displays the voltage of the control input ( $V_{ctrl}$ ), which remains constant, verifying that the VCO output attains a stable state in relation to the specified control voltage.

### DC Analysis:

In the DC analysis, the graph on the right illustrates the circuit's response to various DC voltages applied to the control voltage input. The top graph displays a linear correlation between the input control voltage ( $V_{ctrl}$ ) and the output voltage of the VCO, as anticipated. This indicates that as the control voltage rises from 0 to 5 V, the output voltage experiences a predictable variation, verifying the linear characteristics of the VCO in the DC operating range. The lower graph depicts the control voltage at a specific point, demonstrating a notable change in the output voltage as the control voltage is introduced, confirming that the VCO operates as expected with the control voltage influencing the output in a standard manner.

The transient analysis shows how the VCO stabilizes and oscillates over time, while the DC analysis confirms the expected linear relationship between control voltage and output voltage.

### Advantages of VCO:

- VCOs can operate over a wide range of frequencies, from a few kilohertz to several gigahertz.
- VCOs can produce square waves, triangular waves, or sine waves, depending on the application.
- VCOs are a key component of PLLs, which are control systems that generate a signal with a fixed relation to the phase of a reference signal
- Low Power Consumption
- VCOs can be integrated into compact circuits, enabling smaller overall system designs
- Precision and Stability
- By eliminating voltage fluctuations, voltage regulators reduce energy waste and promote energy efficiency, resulting in cost savings on electricity bills.

### Application of VCO:

- **Frequency Synthesis:** VCOs are commonly used in frequency synthesizers to generate precise frequencies. By varying the control voltage, they can generate a wide range of output frequencies. This makes them essential in applications like radio transmitters, receivers, and communication systems.
- **Phase-Locked Loops (PLLs):** VCOs are a fundamental component of PLLs, which are used for frequency stabilization and signal synchronization. The PLL adjusts the frequency of the VCO to match a reference signal, enabling clock generation, demodulation, and frequency multiplication in systems like radios, TV transmitters, and data communication systems.
- **FM Modulation:** VCOs are used for frequency modulation (FM) in communication systems. The frequency of the VCO is varied according to the input signal, enabling the transmission of information via changes in frequency, as seen in FM radio broadcasting and wireless communication.
- **Signal Generators:** VCOs are used in signal generators for testing and calibration of various electronic systems. They are employed in oscilloscopes, spectrum analyzers, and function generators for producing periodic signals at variable frequencies.
- **Radar Systems:** In radar systems, VCOs are used to generate the **carrier frequency** for transmitting signals. By varying the frequency of the VCO, it helps in frequency hopping, which is essential for reducing interference and improving signal detection in radar and sonar applications.
- **Clock Generation:** VCOs are used to generate clock signals for digital circuits. In systems requiring a precise clock, VCOs can generate a stable and adjustable frequency. They are used in microprocessors, digital signal processors (DSPs), and FPGA designs.
- **Audio Systems:** VCOs are used in audio applications for generating tones or audio signals with tunable frequencies. They are commonly found in synthesizers, sound generators, and audio signal processors.
- **Test and Measurement Equipment:** VCOs are used in test equipment such as signal analyzers and signal generators to produce variable frequency signals for calibrating and testing electronic devices.



### References:

- H. -H. Hsieh and L. -H. Lu, "A High-Performance CMOS Voltage-Controlled Oscillator for Ultra-Low-Voltage Operations," in IEEE Transactions on Microwave Theory and Techniques, vol. 55, no. 3, pp. 467-473, March 2007, doi: 10.1109/TMTT.2006.891471.
- J. Kim, T. -K. Jang, Y. -G. Yoon and S. Cho, "Analysis and Design of Voltage-Controlled Oscillator Based Analog-to-Digital Converter," in IEEE Transactions on Circuits and Systems I: Regular Papers, vol. 57, no. 1, pp. 18-30, Jan. 2010, doi: 10.1109/TCSI.2009.2018928.
- A. Dec and K. Suyama, "Microwave MEMS-based voltage-controlled oscillators," in IEEE Transactions on Microwave Theory and Techniques, vol. 48, no. 11, pp. 1943-1949, Nov. 2000, doi: 10.1109/22.883875.
- S. Radha, D. S. Shylu, P. M. S. Sanchana, C. Dianna, T. Aishwarya and H. S. Selvamani, "Transformer Coupled Voltage Controlled Oscillator Using 180nm Technology in Cadence Tool," 2019 2nd International Conference on Signal Processing and Communication (ICSPC), Coimbatore, India, 2019, pp. 173-177, doi: 10.1109/ICSPC46172.2019.8976679.
- A. Vatsh, "Efficient Voltage-Controlled Oscillator Architecture for High-Frequency Applications," 2024 15th International Conference on Computing Communication and Networking Technologies (ICCCNT), Kamand, India, 2024, pp. 1-6, doi: 10.1109/ICCCNT61001.2024.10724840.
- S. S. Susan and S. S. Yellampalli, "Design of a High Speed PLL using LC VCO in a 180nm CMOS technology," 2021 2nd International Conference for Emerging Technology (INCET), Belagavi, India, 2021, pp. 1-5, doi: 10.1109/INCET51464.2021.9456374.
- E. Shirley Jesseca, K. K. Abdul Majeed and V. Vijayvargiya, "Design and Implementation of Transmission Gate based VCO Architectures for Better Performance," 2022 7th International Conference on Communication and Electronics Systems (ICCES), Coimbatore, India, 2022, pp. 1-5, doi: 10.1109/ICCES54183.2022.9835834.
- I. D. Psycharis, V. Tsourtis and G. Kalivas, "A 30 GHz Class-C Switchless Dual-Band Two Core VCO in 40-nm CMOS," 2024 13th International Conference on Modern Circuits and Systems Technologies (MOCASST), Sofia, Bulgaria, 2024, pp. 01-04, doi: 10.1109/MOCASST61810.2024.10615525.

### **Conclusion:**

In summary, utilizing a Voltage-Controlled Oscillator (VCO) with Cadence Virtuoso presents an effective and powerful method for designing and simulating VCO circuits across multiple applications. Cadence offers a strong platform for developing accurate VCO designs, allowing users to investigate various oscillator configurations, enhance performance, and assess key factors such as frequency stability, power usage, and sensitivity to control voltage.

By employing Cadence's resources, including schematic capture, simulation (Transient and DC Analysis), and layout generation, engineers can model the VCO's performance, confirm its functionality, and refine its design for practical applications like frequency synthesis, PLL circuits, FM modulation, and signal generation. Furthermore, Cadence facilitates the assessment of performance indicators such as phase noise, tuning range, and linearity, ensuring the VCO complies with the necessary standards for its designated purpose.

In conclusion, Cadence supports a thorough and efficient approach to VCO implementation, from idea development to validation, establishing it as an essential instrument for creating high-performance VCOs for communication, signal processing, and a variety of other electronic systems.